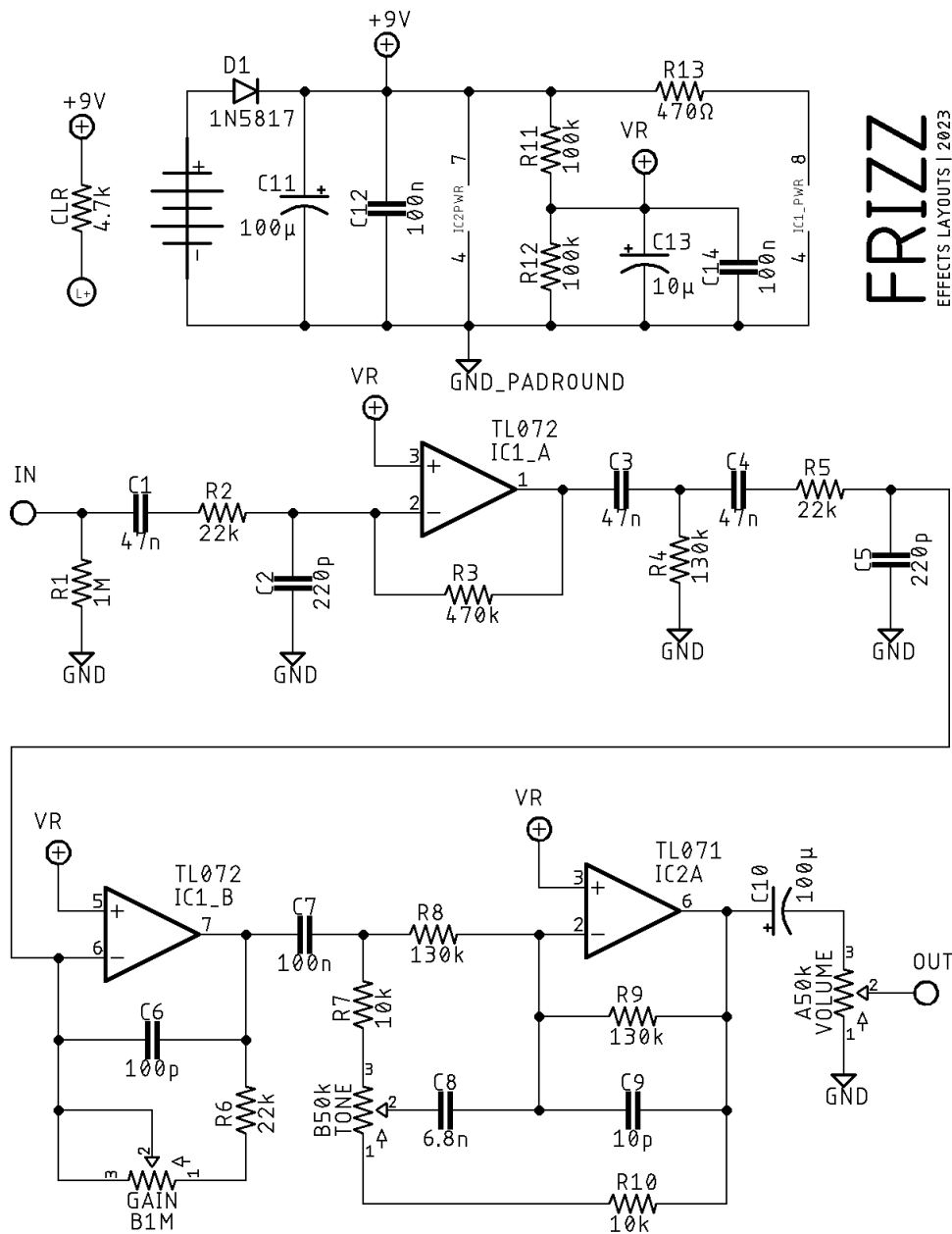


# FRIZZ

## DESCRIPTION

The FRIZZ is an op amp-based fuzz based on the EWS Fuzzy Drive. The cascaded gain stages allow you to dial in a variety of tones from warm overdrive to buzzy fuzz tones. See notes below following the BOM for suggested mods.

## SCHEMATIC



**FRIZZ**  
EFFECTS LAYOUTS | 2023

## BOM

### Resistors

R1	1M
R2	22k
R3	470k
R4	130k
R5	22k
R6	22k
R7	10k
R8	130k
R9	130k
R10	10k
R11	100k
R12	100k
R13	470Ω
CLR	4.7k

### Capacitors

C1	47n
C2	220p
C3	47n
C4	47n
C5	220p
C6	100p
C7	100n
C8	6.8n
C9	10p

C10	100μ
C11	100μ
C12	100n*
C13	10μ
C14	100n*

\*ceramic

### Semiconductors

D1	1N5817
IC1	TL072
IC2	TL071

### Electromechanical

Gain	B1M
Tone	B50k
Volume	A50k

### Notes


This circuit is ripe for modification, so use sockets on caps like C1, 3-4, 7-8, as well as the op amps. I'm wondering what an LM308N might sound like for IC2 (though you'd need to add a 30p cap from pins 1-8. And if you want less gain, try using a lower value gain pot and/or lower the value of R3.

## SHOPPING LIST


Value	Type (suggested)	Quantity
470Ω	¼ watt metal or carbon film	1
4.7k	¼ watt metal or carbon film	1
10k	¼ watt metal or carbon film	2
22k	¼ watt metal or carbon film	3
100k	¼ watt metal or carbon film	2
130k	¼ watt metal or carbon film	3
470k	¼ watt metal or carbon film	1
1M	¼ watt metal or carbon film	1
10p	Ceramic	1
100p	Ceramic	1
220p	Ceramic	2
6.8n	Film	1
47n	Film	3
100n	Film	1

100n	Ceramic	2
10μ	Electrolytic (25v+)	1
100μ	Electrolytic (25v+)	2
1N5817	Schottky rectifier diode	1
TL071	Single op-amp	1
TL072	Dual op-amp	1
A50k	16mm right angle PC mount	1
B50k	16mm right angle PC mount	1
B1M	16mm right angle PC mount	1


LAYOUT

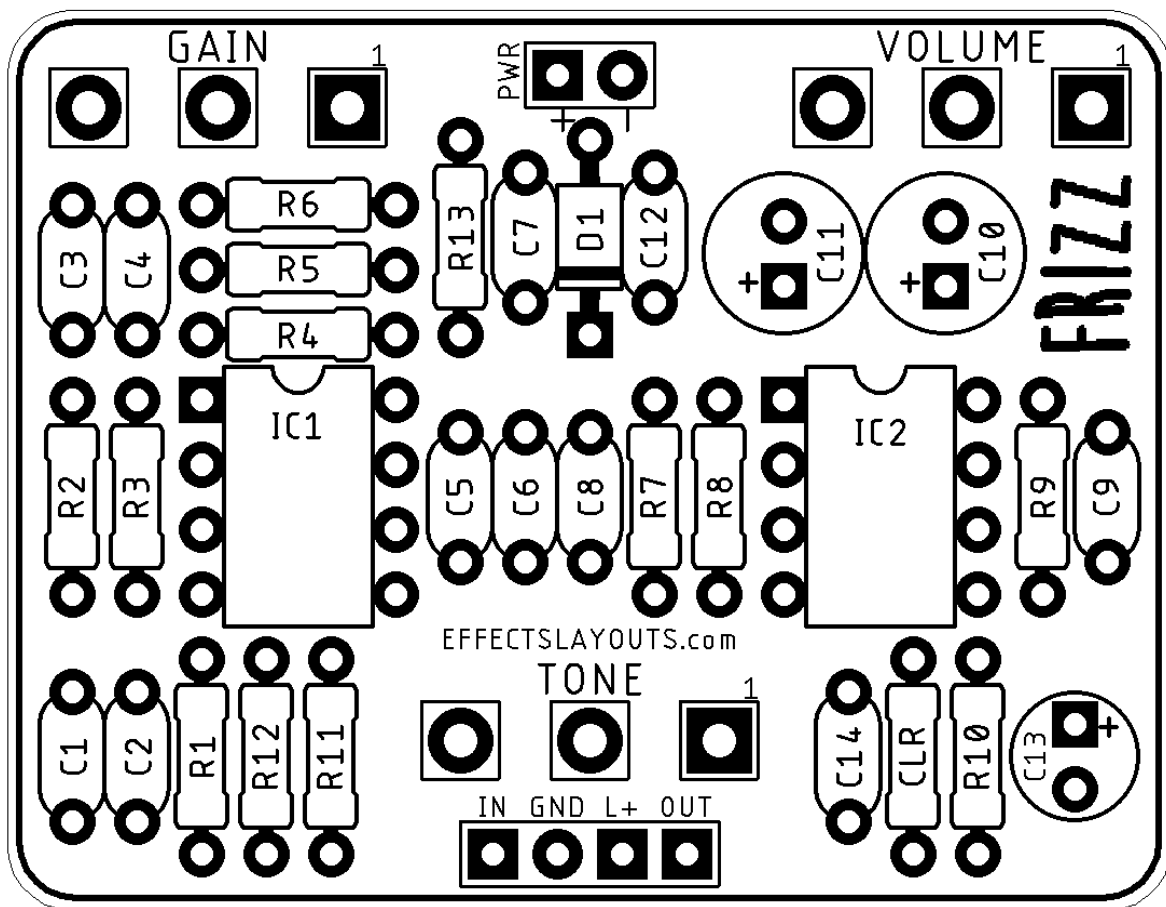

**DRILL TEMPLATE (1590B)**

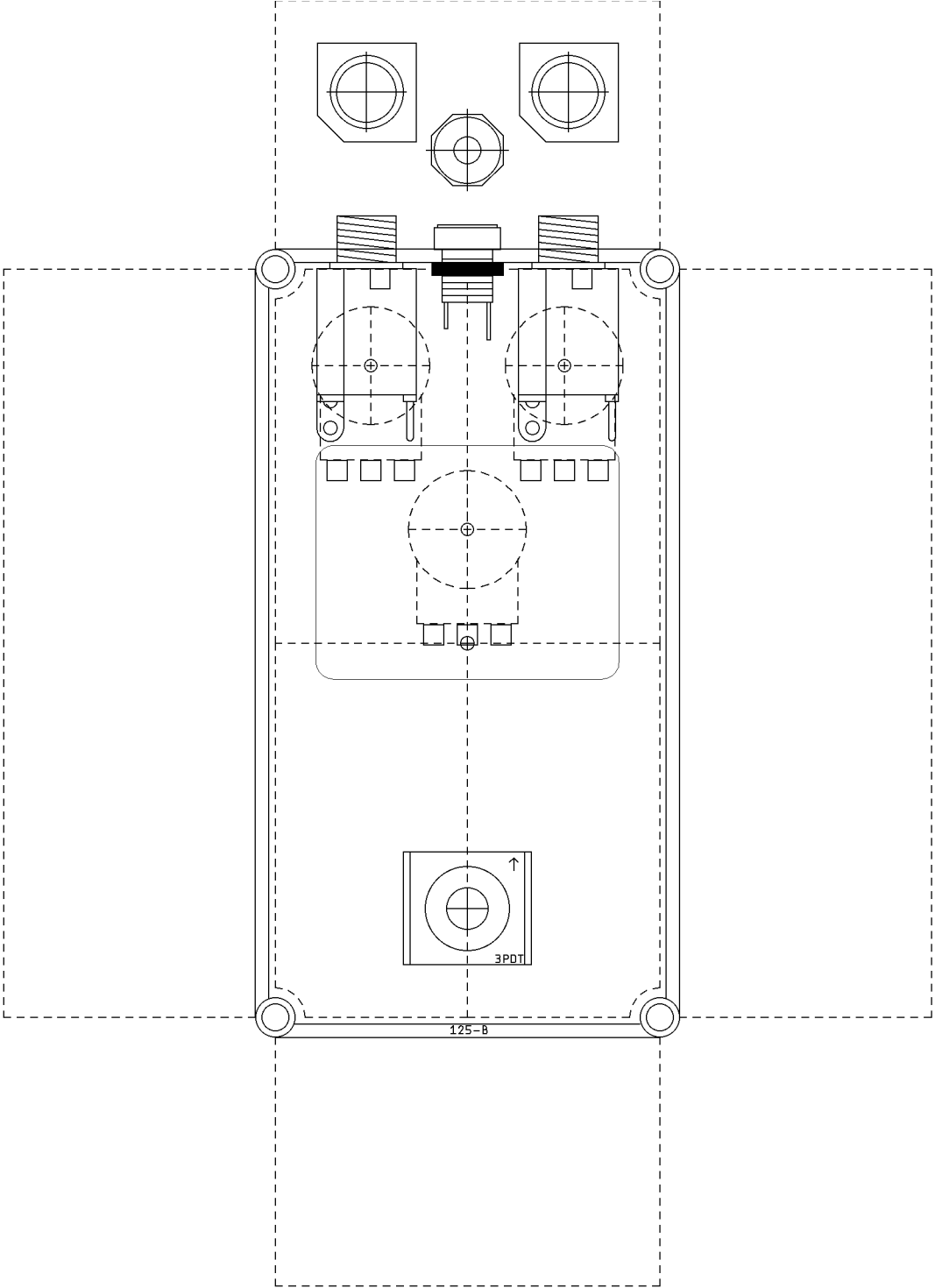

**DRILL TEMPLATE (1590B)**

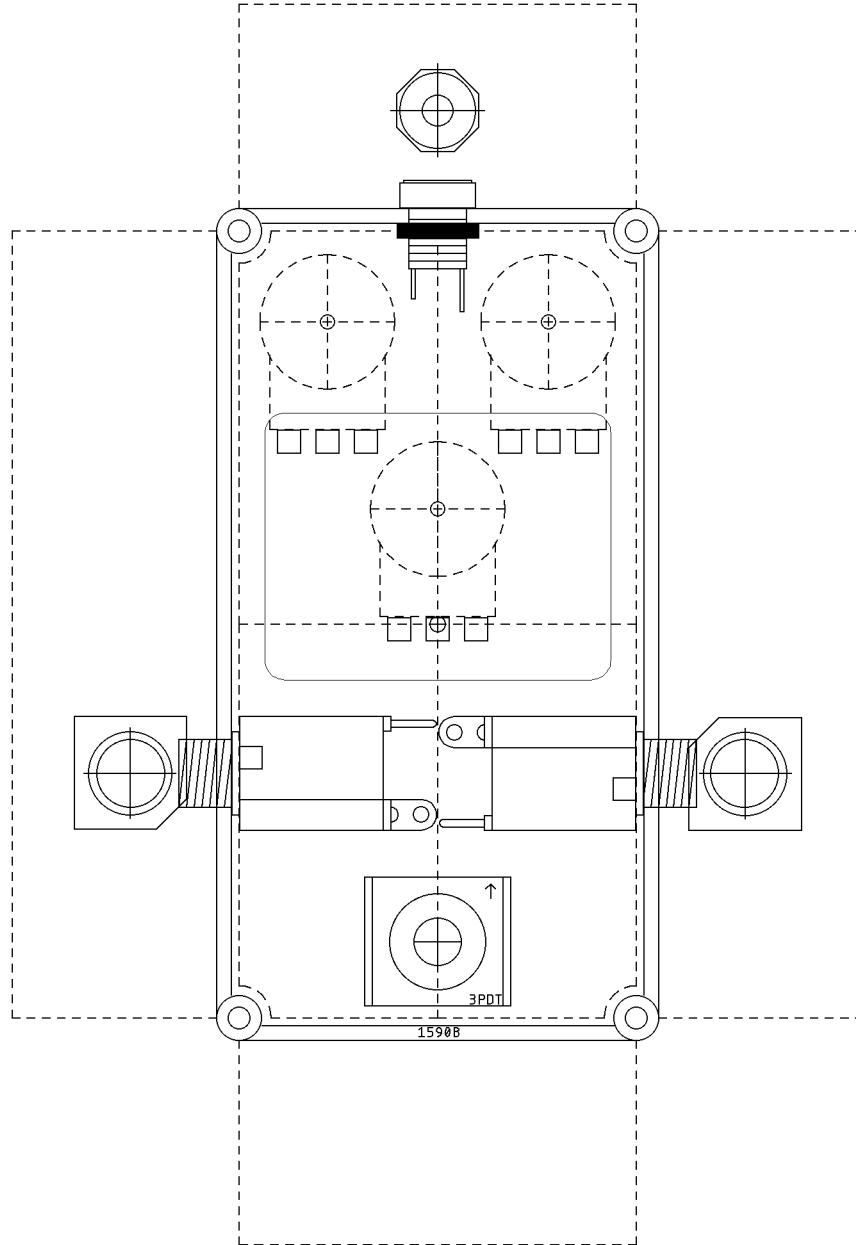

EFFECTS LAYOUTS © 2023  
For DIY and small commercial applications.  
Not for non-peer to peer resale.